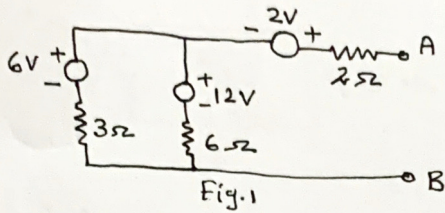


SELECTED PROBLEMS ON CIRCUIT THEORY (EE-212)


- ① Reduce the network of fig.1 to a single voltage source and with a series resistance at terminal A-B.

[Ans. 10V, 4Ω]




- ② The impedance across the terminal A-B as shown in fig.2 is to be a pure resistance of 500Ω at $f = \frac{10^5}{2\pi}$ Hz. Determine L and C.

[L = 2mH ; C = 0.01μ]

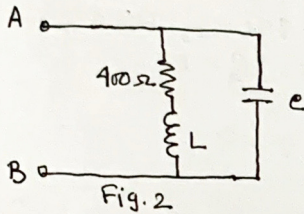


- ③ Find out the conditions under which the power factor of the circuit shown in fig.3 will be unity at all frequency.

[Ans. $R_1 = R_2$ and $L = CR_1^2$]

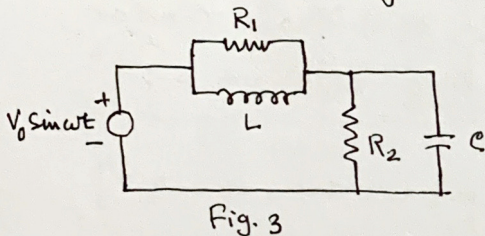

- ④ Convert the current sources into equivalent voltage sources in fig.4 and find out V_0 .

[Ans. 2 Volt]

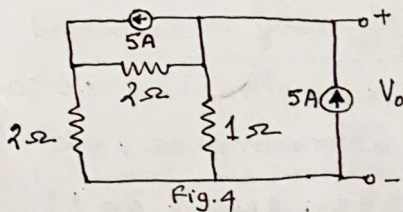

- ⑤ A parallel RLC circuit is required to have resonance at 1000 rad/sec. The impedance at resonance is 10^5 ohm and the bandwidth is 100 rad. Determine R, L and C values.

[Ans. $R = 990\Omega$, $L = 9.9\mu$, $C = 0.1\mu F$]

- Find out the resonant frequency of the circuit shown in Fig. 5
 If $v(t) = 2 \sin t$ volt then find out $i(t)$.

[Ans. 1 rad/sec , $i(t) = 1.6 \sin t \text{ A}$]

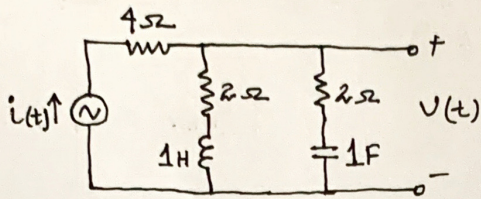


Fig. 5

- Find out the resonant frequency, 3dB bandwidth and Q-factor at resonance of the circuit shown in Fig. 6.

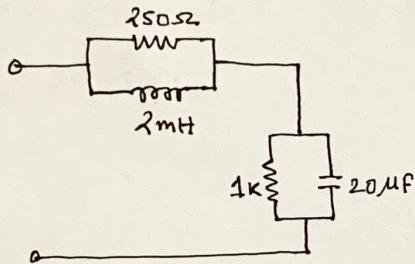


Fig. 6

[Ans. $f_r = 796 \text{ Hz}$, $BW = 39.8 \text{ Hz}$,
 $Q = 20$]

- A coil of inductance L and resistance R is in shunt with a capacitor C . The driving point impedance $Z(s)$ has a zero at $s = -1/2$ and poles at $(-1/4 \pm j \frac{\sqrt{15}}{4})$. Also $Z(j0) = 1 \Omega$. Calculate the values of R , L and C .

[Ans. $R = 1 \Omega$, $L = 2 \text{ H}$, $C = 1/2 \text{ F}$]

[Hint. X_L of inductor $= j\omega L = sL$ and $X_C = 1/j\omega C = 1/sC$]
 $Z(s)$ is the impedance represented in s -domain.

- A 100 volt (peak value) source with variable frequency is connected to a series RLC circuit with $R = 50 \Omega$, $L = 0.5 \text{ H}$, and $C = 50 \mu\text{F}$. Determine the resonant frequency, current at resonance, and Q-factor.

[Ans. 31.83 Hz , 2 Amp. , $Q = 2$]

- Determine the frequency at which the voltage V_o shown in Fig. 7 will be zero.

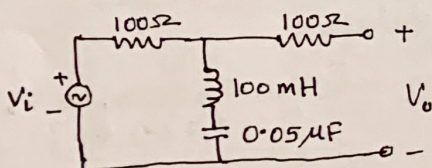


Fig. 7

[Ans. 2.25 KHz]

Transform the voltage sources of fig. 8 into equivalent current sources and find out the current through R_L .

[Ans. Current through R_L is 1]

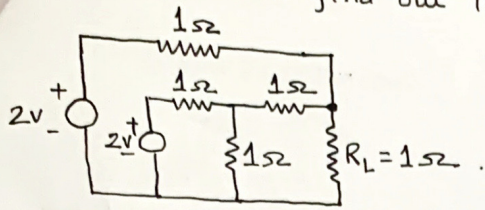


Fig. 8

12) Find out the voltage V_{AB} of the fig. 9 network.

[Ans. $V_{AB} = 75.2 \angle 55.2^\circ$ V]

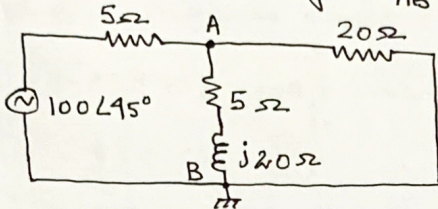


Fig. 9

13) Calculate the current 'I' in the circuit shown in fig. 10.

[Ans. 1 Amp]

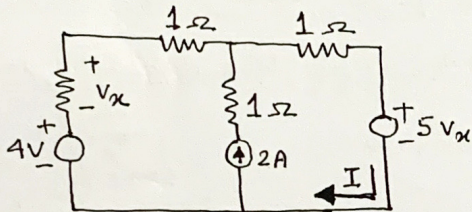


Fig. 10

14) Determine the value of source voltage of the fig. 11.

[Ans. $V = 4.04$ Volt]

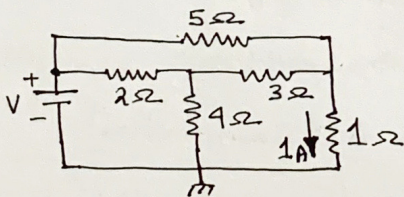


Fig. 11

15) Find out the voltage V_x of the circuit shown in fig. 12

[Ans. $V_x = \frac{4}{9}$ Volt]

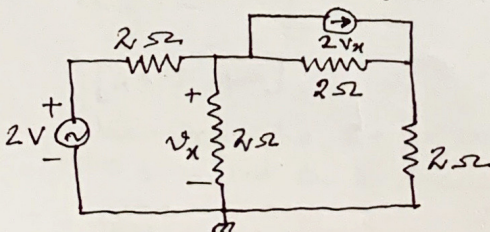


Fig. 12

- ⑥ Find out the power delivered to the dependent voltage source shown in fig. 13.

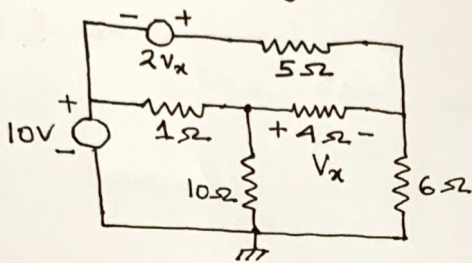


Fig. 13

[Ans. -2.337 watt]

- ⑦ Find out the current 'I' in the circuit shown in fig. 14.

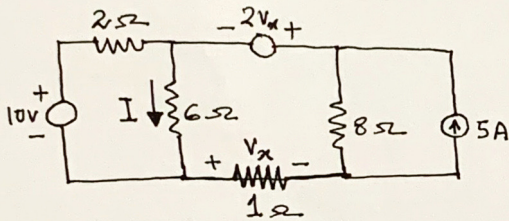


Fig. 14

[Ans. $I = 1.9 \text{ Amp}$]

- ⑧ Determine the value of the capacitor 'c' as shown in fig. 15, for maximum power transfer to the load 10Ω .

[Ans. $50\mu\text{F}$]

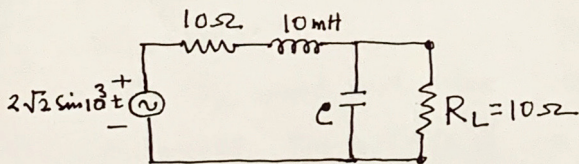


Fig. 15

- ⑨ Find out the R_{in} of the circuit shown in fig. 16.

[Ans. 4.37Ω]

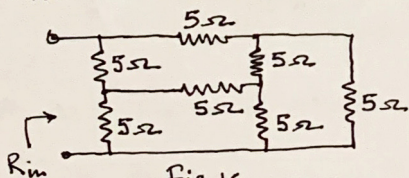


Fig. 16

[Hint: Use Δ -Y transformation]

- ⑩ Determine the current through the resistance $R_L = 1\Omega$ of fig. 17.

[Ans. 0.4 A]

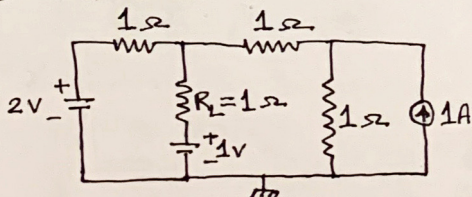


Fig. 17

Find out the value of R_L in the circuit shown in fig.18 for maximum power delivered to it.

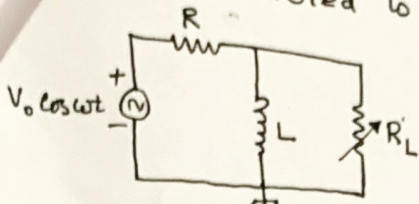


Fig. 18

[Ans. $R_L = R\omega L / \sqrt{R^2 + \omega^2 L^2}$]

22

Find out the impedance faced by the voltage source 'V' in the circuit shown in fig.19.


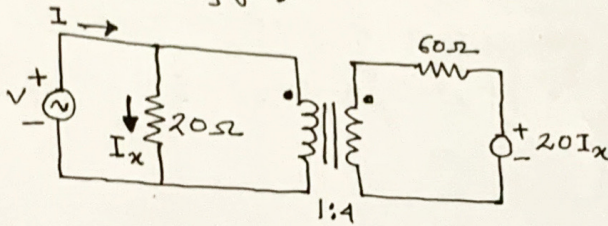


Fig. 19


[Ans. 4Ω]

23

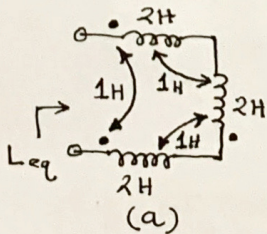What will be equivalent mutual inductances of the circuits shown in fig.20(a) and fig.20(b)?



(a)

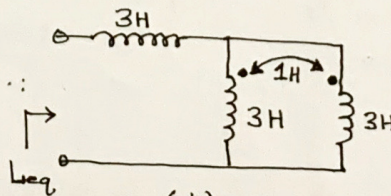

(b)

Fig. 20

[Ans. (a) $4H$, (b) $5H$]

24

Determine the voltages V_1 , V_2 , and V_3 with respect to the ground as shown in fig.21

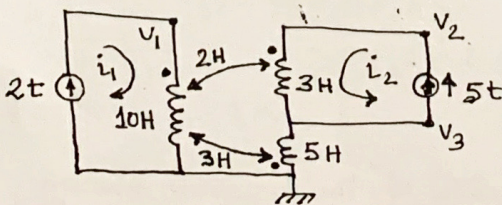


Fig. 21

[Ans. $V_1 = 30V$, $V_2 = 25V$, $V_3 = 6V$]

25

Determine the Z-parameters of the network shown in fig.22.

Also find out the Y-parameters using the relation between Y and Z parameters

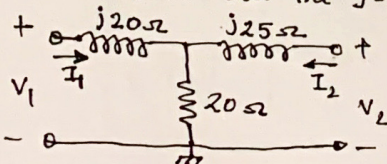


Fig. 22

[Ans. $Z_{11} = (20 + j20)\Omega$, $Z_{12} = 20\Omega$
 $Z_{21} = 20\Omega$; $Z_{22} = (20 + j25)\Omega$
 $Y_{11} = 0.031 \angle 112.28^\circ S$, $Y_{12} = Y_{21} = 0.019 \angle 60.94^\circ S$
 $Y_{22} = 0.027 \angle 105.94^\circ S$]

- 26) Find out the h-parameters of the network shown in fig. 23.

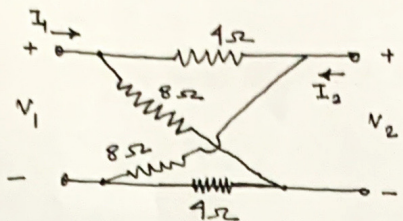


Fig. 23

$$\begin{bmatrix} h_{11} = \frac{14}{3} \Omega ; h_{12} = \frac{1}{3} \text{ V} \\ h_{21} = -\frac{1}{3} ; h_{22} = \frac{1}{6} \Omega^{-1} \end{bmatrix}$$

- 27) Find out y-parameters as well as z-parameters of the network shown in fig. 24.

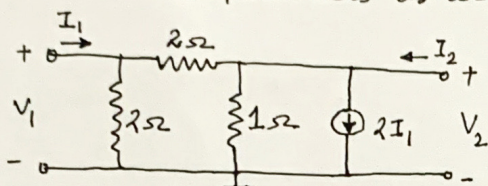


Fig. 24

$$\begin{bmatrix} \text{Ans. } y_{11} = 1 \Omega^{-1} ; y_{12} = -0.5 \Omega^{-1} ; y_{21} = 1.5 \Omega^{-1} ; y_{22} = 0.5 \Omega^{-1} \\ z_{11} = \frac{2}{5} \Omega ; z_{12} = \frac{2}{5} \Omega ; z_{21} = -\frac{6}{5} \Omega ; z_{22} = \frac{4}{5} \Omega \end{bmatrix}$$

- 28) Find out the z-parameters of the network shown in fig. 25.

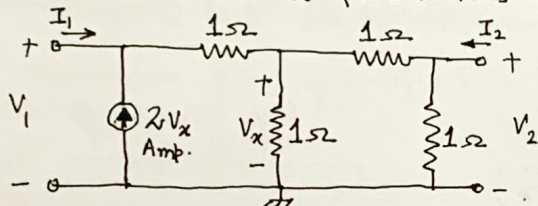


Fig. 25

$$\begin{bmatrix} \text{Ans. } z_{11} = -5 \Omega ; z_{12} = -3 \Omega \\ z_{21} = -1 \Omega ; z_{22} = 0 \end{bmatrix}$$

- 29) Determine the h-parameters of the network shown in fig. 26

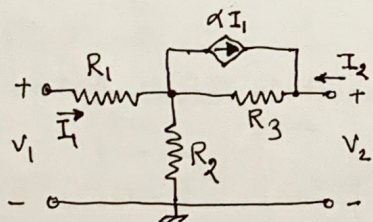


Fig. 26

$$\begin{bmatrix} \text{Ans. } h_{11} = R_1 + [(1-\alpha)R_2R_3/(R_2+R_3)] \\ h_{12} = R_2/(R_2+R_3) \\ h_{21} = -(\alpha R_3+R_2)/(R_2+R_3) \\ h_{22} = 1/(R_2+R_3) \end{bmatrix}$$

- 30) Find out the y-parameters and z-parameters of the network shown in fig. 27.

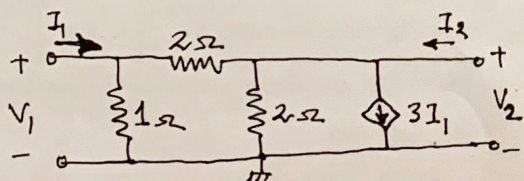


Fig. 27.

$$\begin{bmatrix} \text{Ans. } \begin{bmatrix} -0.4 & 0.4 \\ -3.2 & 1.2 \end{bmatrix} = [Z] \\ \begin{bmatrix} 1.5 & -0.5 \\ 4 & -0.5 \end{bmatrix} = [Y] \end{bmatrix}$$